

CPS1 KICK HARNESS

Spare parts

opur o pur to		
Connector	H10P-SHF-AA - 10 Pin Female connector	
	aka JST-NH 10 Female connector	
Pins	SHF-001T-0.8BS Female	
	aka JST NH PIN Female	
Wire	22 AWG as per JST recommendation	

Pinout for 6 buttons games

Wire colors	Pin number	Connections
Black	1	GND
Black	2	GND
Purple	3	Player 1 button 4
Gray	4	Player 1 button 5
White	5	Player 1 button 6
	6	NC A.O.
Orange	7	Player 2 button 4
Green	8	Player 2 button 5
Blue	9	Player 2 button 6
	10	NC

Pinout for 3/4 player games				
Wire colors	Pin number	Connections		
Black	1	GND		
Black	2	GND		
6	3	Right		
COL	4	Left		
	5	Down		
	6	Up		
	7	Button 1		
NA.	8	Button 2		
W.	9	Coin		
	10	Start		

Pictures







SHF-001T-0.8BS



WIRE 22 AWG



CONNECT 6 BUTTONS

Spare parts

Terminals	12 * 2.8mm Crimp Terminals Female Spade Connec	tor
Ground	Use Standard Female Terminals	
	or Crimp Closed End Connectors	ON
Enclosure	Quick Disconnect Sleeve	24.00
Optionnal	or Quick Disconnect Enclosure	THE !
How to connect to buttons? Using Ground wire in the same connector		
osing dround	PLAYER 1 - BUTTON 4	
	GROUND 1	

How to connect to buttons?


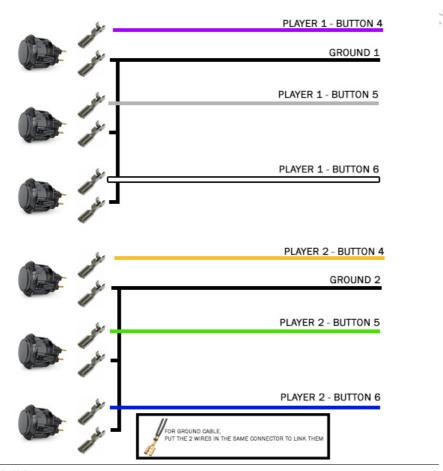


Figure a

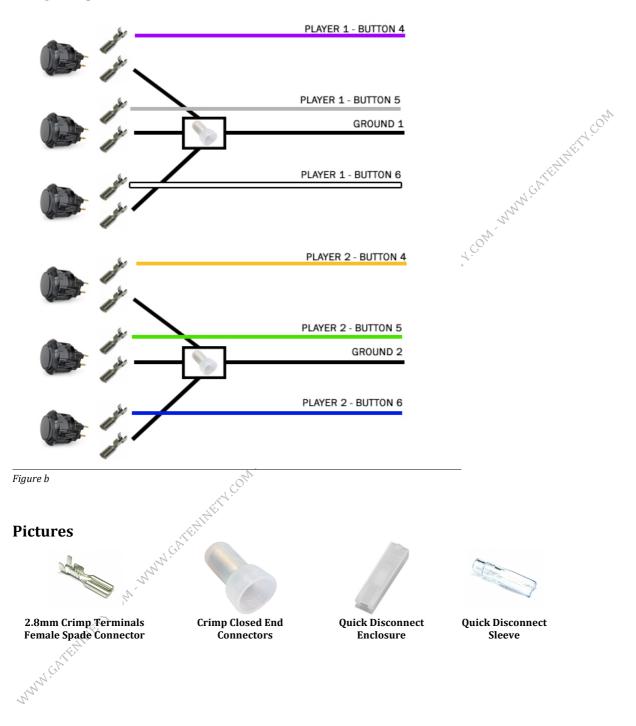

Using crimp closed end connectors





CONNECT 3 OR 4 PLAYER

Spare parts if using microswitches with 4.8 terminals

spare parts it asing interest with the terminals		
Terminals	8 * 4.8mm Crimp Terminals Female Spade Connector	
	and 8 * 2.8mm Crimp Terminals Female Spade Connector	
Ground	Use Standard Female Terminals	
	or Crimp Closed End Connectors	
Enclosure	2.8mm Quick Disconnect Sleeve / 2.8mm Quick	
Optionnal	Disconnect Enclosure for 2.8mm Crimp Terminals Female	
	Spade Connector	
	and 4.8mm Quick Disconnect Sleeve for 4.8mm Crimp	
	Terminals Female Spade Connector	

$How \ to \ connect \ the \ buttons \ and \ joystick \ ?$

Using Ground wire in the same connector

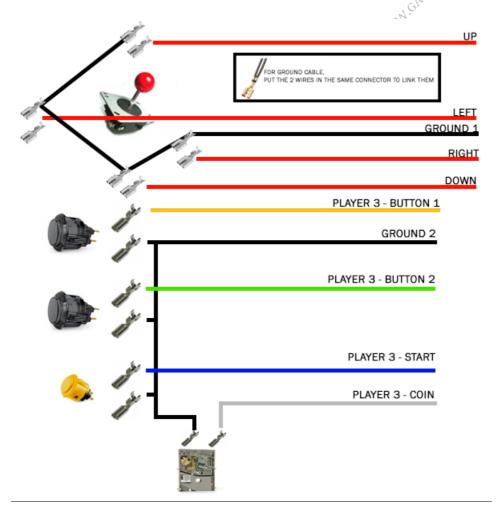


Figure C



Using crimp closed end connectors

The only difference with « figure c » is the ground wire using Crimp Closed End Connectors instead of linking them via the female terminals. Please refer to « figure b » for the principle.



SANWA / SEIMITSU

Are you using the 5-pin wire harness for joytick?

